

McGILL UNIVERSITY

ECSE 325

DIGITAL SYSTEMS

Lab 1 Report

Authors (Group 07):

John Wu

Ege Ozer

Student Number:

260612056

260688342

March 2, 2018

Contents

1	Introduction	2
2	VHDL Code	2
3	Compilation Report	2
4	Resource Utilization	3
4.1	Chip Planner	4
4.2	RTL View	4
5	Conclusion	5

1 Introduction

The goal of the following lab is to learn the basics of the Quartus-II FPGA software as well as how to compile the synchronous circuit VHDL declarations to a target FPGA. We will also be looking at how the fitter of the Quartus compiler maps the design to the FPGA hardware. In order to do so, we will be going through the process of making an 8-bit counter which has functions for counting up, counting down, and resetting.

2 VHDL Code

See attached g07_lab1.file for the VHDL code that implements the 8-bit counter.

3 Compilation Report

Tasks			Compilation	Flow Summary	
	Task	Time			
✓	▼ ▶ Compile Design	00:01:30		Flow Status In progress - Mon Feb 19 16:52:14 2018	
✓	> ▶ Analysis & Synthesis	00:00:16		Quartus Prime Version 16.1.0 Build 196 10/24/2016 SJ Lite Edition	
✓	> ▶ Fitter (Place & Route)	00:00:45		Revision Name g07_lab1	
✓	> ▶ Assembler (Generate programming files)	00:00:13		Top-level Entity Name g07_lab1	
✓	> ▶ TimeQuest Timing Analysis	00:00:12		Family Cyclone V	
✓	> ▶ EDA Netlist Writer	00:00:04		Device 5CSEMA5F31C6	
	■ Edit Settings			Timing Models Final	
	🔧 Program Device (Open Programmer)			Logic utilization (in ALMs) N/A	
				Total registers 8	
				Total pins 12	
				Total virtual pins 0	
				Total block memory bits 0	
				Total DSP Blocks 0	
				Total HSSI RX PCSs 0	
				Total HSSI PMA RX Deserializers 0	
				Total HSSI TX PCSs 0	
				Total HSSI PMA TX Serializers 0	
				Total PLLs 0	

Shown above on the left is our successful compilation report. On the right, we have a flow summary of the compilation. We can see from the summary that the design was successfully uploaded to the 5CSEMA5F31C6 device that is part of the Cyclone V family. In addition, we can notice that a summary of the resource utilization in the report which will be described in the next section.

4 Resource Utilization

From the RTL-viewer we observe that we have three 2X1 Multiplexers(MUX), two adders and one D-flipflop. More precisely with the flowchart above, it states that our design uses a total of 12 registers and 8 pins. we can think of few possibilities that might cause more resources to be used than it should when we back-track the implementation of our design.


Our design's 8-bit counter variable is using 2^n integers where n represents the amount of bits used as a way of storing the values. Although it sounds logical, this decision might be problematic as it may take more resources. For instance, an 8 bit counter requires a signal with a range $[0, 255]$ to store $2^8 = 256$ numbers. Now to put into perspective, suppose we have a 32-bit counter, this would imply that we would require $2^{32} = 4294967296$ values for own counter signal.

Additionally, since the output is declared using `STD_Logic_Vector`, we need to convert it to unsigned type in order to prevent compilation errors. However, this might have caused additional resources and overhead for our 8-bit counter. We presume that the overhead will increase exponentially with the increase of the bit size of the counter.

If we could re-design our 8-bit counter, we would use only `STD_Logic_Vector` for the counter variable. This would make future designs and higher bit counters more practical and more efficient to implement. n-bit counters would only require a range of $[0, n-1]$ instead of $[0, 2^n-1]$. As a result, this fix would also get rid of type casting conversion and the use of `IEEE.NUMERIC_STD.ALL` that might create an unnecessary overhead.


To summarise, the resource utilization could be improved by using only `STD_Logic` type variables which would also get rid of overhead.

4.1 Chip Planner

 

Chip planner screenshot, with used resources highlighted.

4.2 RTL View

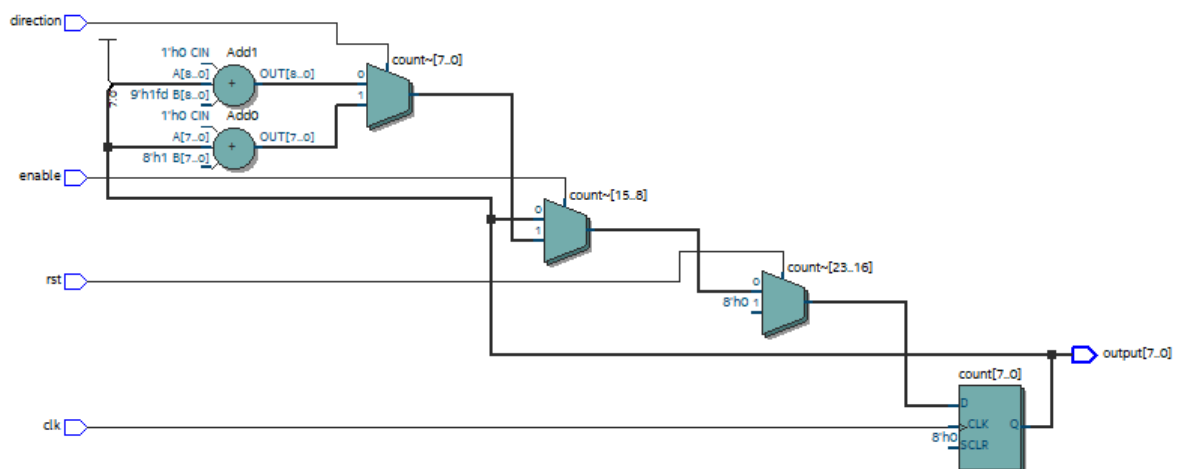

RTL view of the circuit, with description of resource

5 Conclusion

By completing this lab, we have covered the basics of using an FPGA software and learning how to debug code that is written in a hardware description language. In this particular experiment, very few resources were needed to implement our 8-bit counter in the FPGA. However, the techniques learned in this experiment for interpreting the VHDL design will become crucial skills in future labs when the designs become more complex and resource management is crucial.